


PHY 240: Basic Electronics

Homework Problem H12

November 21, 2024
Aiden Rivera

1. What Does it Do?

Consider this circuit:

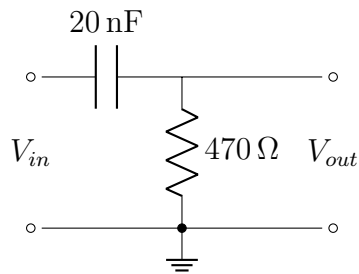


(a) meow!

(b) meow2

Solution: Finding R is easier, so let's do that first.

We know that $V_{in} = 10V$, $V_{out} = 8V$ and our chosen r is $1\text{ k}\Omega$

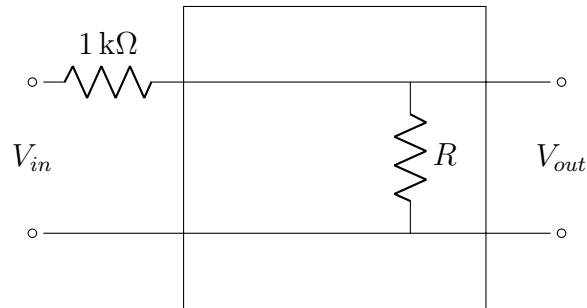At $t = 0$, the capacitor is fully charged, so it acts like an open circuit...



$$V_{in} = I(R_1 + R_2)$$

$$10V = I \cdot 1000\Omega + I \cdot R_2$$

The voltage drop across R_2 is V_{out} which is $8V$, meaning

$$I \cdot 1000\Omega = 2V$$


$$I \cdot R_2 = 8V$$

So $I = 0.002A$, naturally...

$$0.002A \cdot R_2 = 8V$$

$$R_2 = 4\text{ k}\Omega$$

Now, we find C .

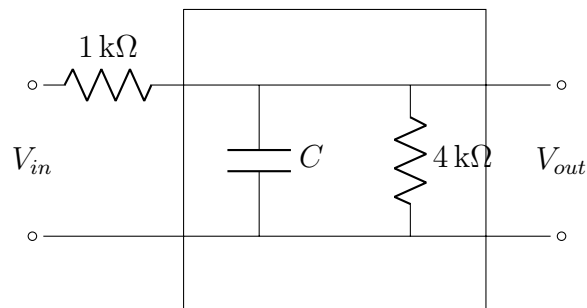

First, we must find R_{eff} which is just the resistances of these resistors in parallel.

$$R_{eff} = 800\Omega$$

The equation $V_{in} \cdot e^{\frac{-t}{RC}}$ tells us the voltage across the capacitor over time. Eyeballing the curve and plugging in known values, we get

$$2.3 = 8 \cdot e^{\frac{-0.0005}{800 \cdot C}}$$

Solving for C now...

$$C = \frac{-0.0005}{800 \cdot \ln \frac{2.3}{8}} \approx 0.5 \mu\text{F}$$